

Seat No. CI-23025

NED UNIVERSITY OF ENGINEERING & TECHNOLOGY
FIRST YEAR (COMPUTER SCIENCE/ GAME & ANIMATION)
SPRING SEMESTER EXAMINATIONS 2024
Batch - 2023

Time: 3 Hours

Dated: 29-07-2024


Max.Marks: 60

LOGIC DESIGN & SWITCHING THEORY - CS-251

Question 1:

(CLO-1 | 12 Marks)

- Show the output of a positive edge triggered JK flipflop the given waveform. Assume the flipflop is initially RESET.
- Differentiate between synchronous & asynchronous counters.
- Give excitation / transition table of SR flipflop.
- Explain race-condition with reference to flipflops?
- Show with the help of a diagram how a 4-bit asynchronous counter can be connected to limit it to form a Mod-10 counter.
- All the flipflops in an asynchronous counter are provided clock inputs. Explain why they are still considered as asynchronous?

 

Question 2:


(CLO-1 | 12 Marks)

- Simplify using Boolean Algebra:
 - $F(W, X, Y, Z) = (WX + W\bar{Y})(W + X) + WX(\bar{X} + \bar{Y})$
 - $F(\overset{X}{A}, \overset{Y}{B}, \overset{Z}{C}) = \overline{(X + \bar{Y}\bar{Z})}(\bar{X}YZ)$
- Elaborate the term 'enable' and elaborate different kinds of enables in an IC?
- Express the following function as a standard sum of minterms and as a standard product of maxterms: $F(A, B, C, D) = C'D + A'B + AD$
- Provide the NAND representation of a XOR gate.
- Consider a 2x1 multiplexer (active high o/p) having select line $S = A$ and data line $D_0 = \bar{B}.C.D$ and $D_1 = \bar{C}.D$. Predict the output of this multiplexer if $A=1, B=1, C=1$ and $D=0$? Show working to support your answer.


Question 3:

(CLO-2 | 12 Marks)

 - Using an active low scheme, you need to create logic for displaying alphabets on a 7-segment display. On inputs 4, 7, 9, 11, 13 and 15, you need to display alphabets U, h, J, n, L and P on the seven-segment display as displayed in the figure below. Customize the circuit for led a and b.



 b. Given figure shows the intersection of Shahrah-e-Faisal(SF) with the Shaheed-e-Millat Road (SM) at Baloch Colony. Vehicle detection sensors are placed along Lanes C & D (SF) and A & B (SM). These sensor outputs are LOW(0) when no vehicle is present and HIGH(1) when a vehicle is present in the lane.



The intersection traffic is to be controlled by the following logic:


- The E-W(east-west) traffic will be green whenever both lanes C and D are occupied.
- The E-W light will be green whenever either C or D is occupied but lanes A and B are not occupied.
- The N-S(north-south) light will be green whenever lanes A and B are both occupied but C and D are both not occupied.
- The N-S light will also be green when either A or B is occupies while C and D are both vacant.
- The E-W light will be green when no vehicle is present.

Using the outputs of sensors A,B,C and D as inputs, **design** a logic circuit that controls the traffic light. There should be two outputs N-S and E-W, which go HIGH when the corresponding light is to be green. Simplify the circuit as much as possible.

Question 4:

(CLO-2 | 12 Marks)

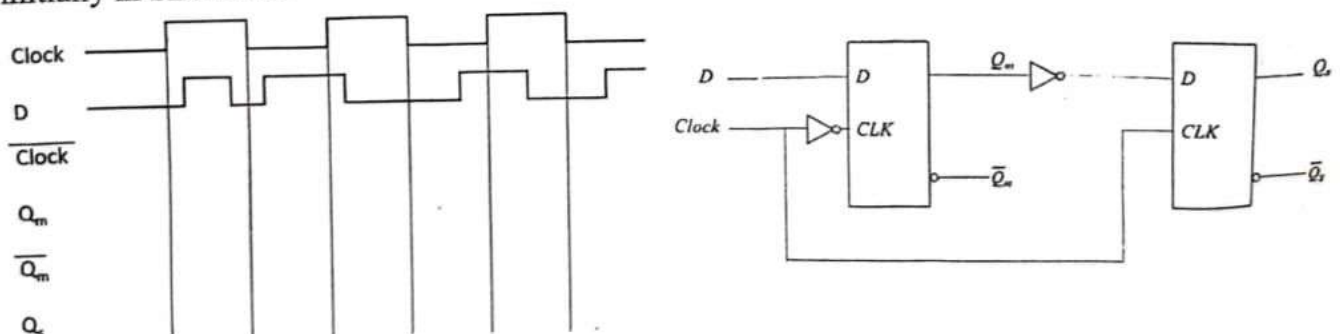- Provide** the characteristic and excitation tables of D flipflop. **Complete** the waveform given in the figure below to show the output of the flipflop. The flipflop is negative edge triggered and is initially in SET state.



- Design** a negative edge triggered Synchronous Mod-8 counter.

Question 5:

(CLO-2 | 12 Marks)

- Cascade half adders to form a 3-bit adder/subtractor. (block diagram only).
- Design a sequential circuit using T flipflop for the state diagram.

