

NED University of Engineering and Technology
Department of Computer Science & Information Technology
FSCS - Midterm Examination Spring 2026
Logic Design and Switching Theory (CS-251)

Paper A

Roll No: [REDACTED]

Time: 90 minutes

Marks: 20

Q1: Answer the following questions:

[CLO-1, Marks 10]

- a. **Perform** subtraction using r's complement :
 - i. $98.7654)_{10} - 987.654)_{10}$
- b. **Demonstrate** by means of truth table the validity of Demorgan's Theorem for 3 input variables.
- c. **Find** the Simplified expression using K-Map for the following function:
 $F(A,B,C,D) = \Sigma(1,3,7,11,15) + d(0,2,5)$
- d. **State** the difference between the following:
 - i. Ripple Carry Adder and Carry Look ahead Adder.
 - ii. Multiplexer and Demultiplexer.

Q2. Design a Full Subtractor Circuit .

[CLO-2, Marks 3]

Q3. Design a 3 to 8 Active LOW enable input line decoder with Active LOW output. Also Show that this circuit is served as 1 x 8 Demultiplexer.

[CLO-2, Marks 3]

Q4. Apply Boolean Algebra to simplify the following expressions: **[CLO-2, Marks 4]**

- i. $X = [A'(B'C)' + A']' + [B(B'C)]'$
- ii. $N = [(X_1' + X_1X_2) + (X_2' + X_1X_2')]'$